

# DE MORGAN'S THEOREMS

[http://www.tutorialspoint.com/computer\\_logical\\_organization/demorgan\\_theroems.htm](http://www.tutorialspoint.com/computer_logical_organization/demorgan_theroems.htm) Copyright © tutorialspoint.com


De Morgan has suggested two theorems which are extremely useful in Boolean Algebra. The two theorems are discussed below.

## Theorem 1


$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

NAND = Bubbled OR

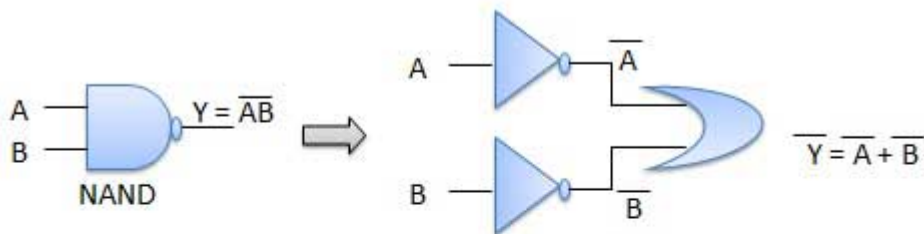- The left hand side *LHS* of this theorem represents a NAND gate with inputs A and B, whereas the right hand side *RHS* of the theorem represents an OR gate with inverted inputs.
- This OR gate is called as **Bubbled OR**.



NAND  $\equiv$  Bubbled OR

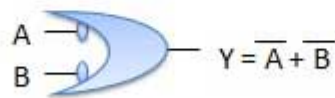

Bubbled OR

Table showing verification of the De Morgan's first theorem –

A	B	$\overline{AB}$	$\overline{A}$	$\overline{B}$	$\overline{A} + \overline{B}$
0	0	1	1	1	1
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	0


## Theorem 2

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$


NOR = Bubbled AND

- The LHS of this theorem represents a NOR gate with inputs A and B, whereas the RHS represents an AND gate with inverted inputs.

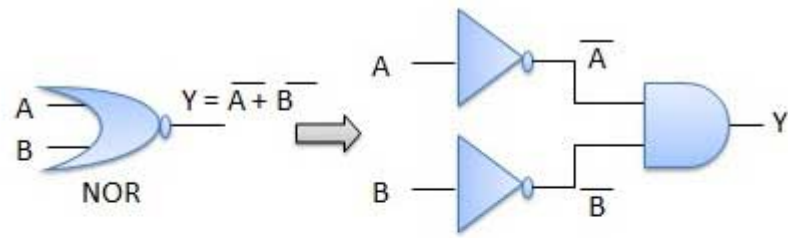- This AND gate is called as **Bubbled AND**.



$\text{NOR} \equiv \text{Bubbled AND}$

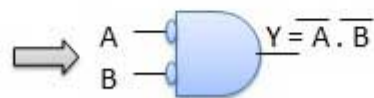

Bubbled AND

Table showing verification of the De Morgan's second theorem –

A	B	$\overline{A+B}$	$\overline{A}$	$\overline{B}$	$\overline{A} . \overline{B}$
0	0	1	1	1	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	0

Loading [Mathjax]/jax/output/HTML-CSS/jax.js